

# MOSFET for Hot-Swap Applications

Author: Shunlong Xiao, Staff Applications Engineer and Peter Wilson, Director Applications Engineering, Alpha and Omega Semiconductor, Inc.  
Date: 05/03/2021

Categories: MOSFETs & Power MOSFETs, Power Semiconductors, Power Supplies

Tag: @AlphaOmega\_Semi #aos #mosfet #psd #powerelectronics


Hot-swap circuits are predominantly used in high-availability systems, such as data centers and telecommunication infrastructure

When hot-swap circuits are used in high-availability systems, the operation will not be interrupted if there is a need to replace or add attentional units for system operation.

Figure 1 shows that hot-swapping can often involve a large transient current (up to hundreds of amperes) to charge the output capacitors, which require a robust MOSFET with a large SOA capability during the linear operating mode. For high power and high redundancy, which are critical in telecom-server applications, a hot-swap controller is needed to regulate the inrush transient current. In telecom-server applications, the backplanes, terminal voltages which


dominate are at 48V and 12V. In typical 12V backplanes, systems are made up of redundant power supplies, and each connected to the parallel hot-swap modules by the O-ring-FETs. The MOSFETs play a key role in the hot-swap application; thus, this article will evaluate the MOSFET behaviors based on 12V ADM1278 hot-swap circuits from ADI.

When the hot-swap module, as shown in Figure 2, is inserted into the 12V backplane, the controller GATE pin will source a constant 24uA  $I_g$  to the MOSFET gate as well as the shunt external  $R_{gate}$  and  $C_{gate}$ . After the GATE voltage reaches the MOSFET threshold  $V_T$ , the  $I_g$  will only charge the external  $C_{gate}$  and MOSFET internal  $C_{rss}$  because the voltage of  $C_{gs}$  across the GATE pin and the  $V_{out}$  node will remain constant. This is similar to the miller-plateau in the switching mode power supply.

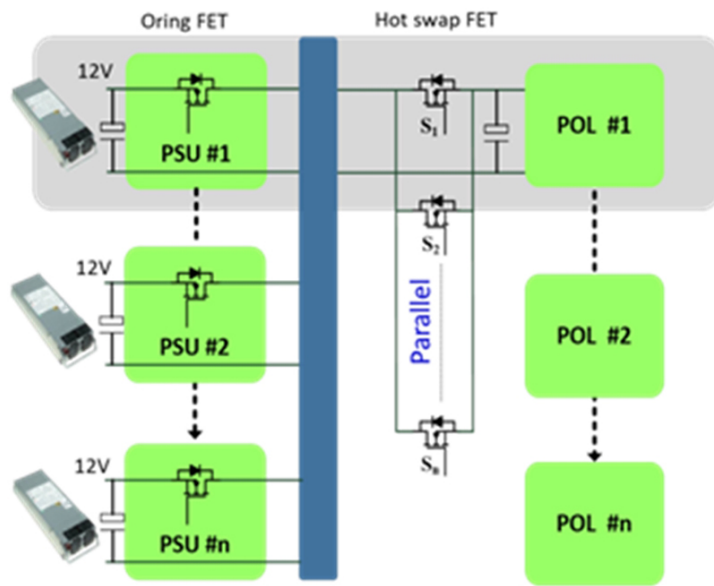

Click image to enlarge

Figure 1. Multi-module Telecom-server Hot-Swap Applications

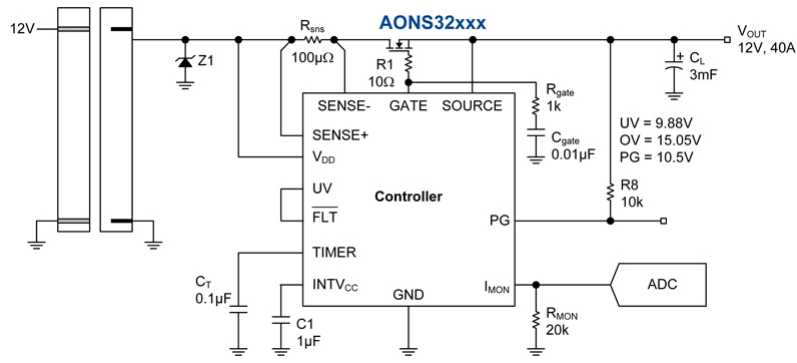

Click image to enlarge


Figure 2. Hot-Swap Circuit Schematic

The inrush current  $I_{in}$  drawn by the output capacitor  $C_L$  can then be expressed as the equation (1,2): Where 'n' stands for the number of MOSFET in parallel.

$$I_{in} = (I_g - nI_{gd}) \frac{C_L}{C_{gate}} + I_{Load}$$


$$I_{gd} = \frac{dQ_{gd}}{dt}$$

Unlike in switching power supplies, where low  $Q_{gd}$  is preferred, larger  $Q_{gd}$  may benefit from lowering inrush current in hot-swap applications. On the other hand, the inrush current is also determined by the number of parallel MOSFETs, the output capacitor  $C_L$  value and the load current. The fewer parallel MOSFETs and the larger output capacitors will lead to larger inrush current stress on the MOSFET. Below are the test waveforms on AOS hot-swap evaluation boards for different scenarios. Figure 3a shows that a larger  $C_L$  will draw a larger inrush current (green curve), while Figure 3b indicates that the increasing number of parallel MOSFETs will decrease the total inrush current (green curve).

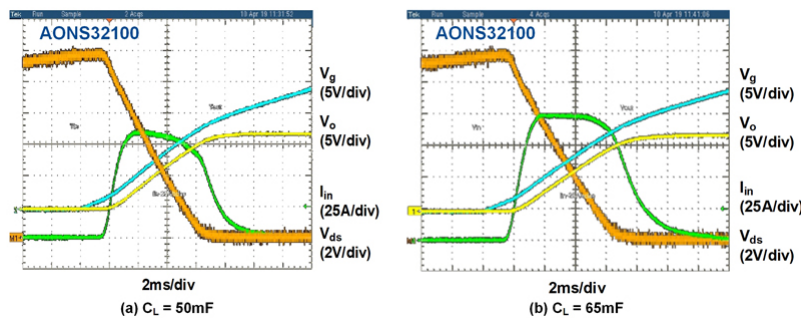

Click image to enlarge

Figure 3a. Comparison of Start-up Waveform with No Load and Different Output  $C_L$

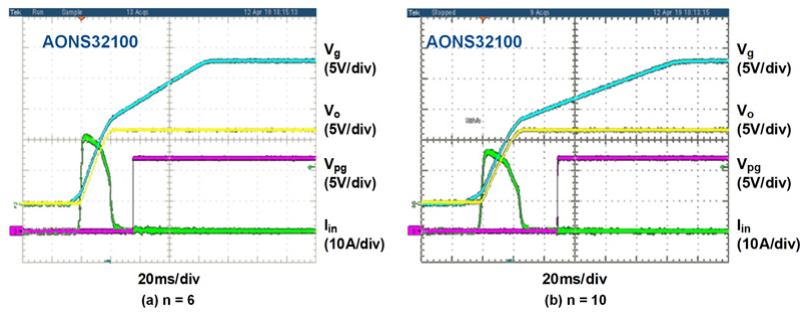


Click image to enlarge

Figure 3b. Comparison of Start-up Waveform with No Load, same  $C_L$  50mF but Different Number of Parallel MOSFET

Telecom-server hot-swap applications involve a large supply current during typical on conditions; therefore, a low  $R_{ds(on)}$  MOSFET is most preferred. A large SOA is required to ensure the system's robustness during start-up and short-circuit conditions when MOSFETs are undergoing high voltage and current stress in linear operation mode.


Figure 4 shows that AONS32310 has a lower inrush current than the competitors because of relatively larger  $C_{rss}$ . This can ease the inrush current limit settings of the system, and the lower  $R_{ds(on)}$  means higher overall efficiency. When the output cap value and input voltage increase, AONS32310 still worked while comparable competitor parts failed.

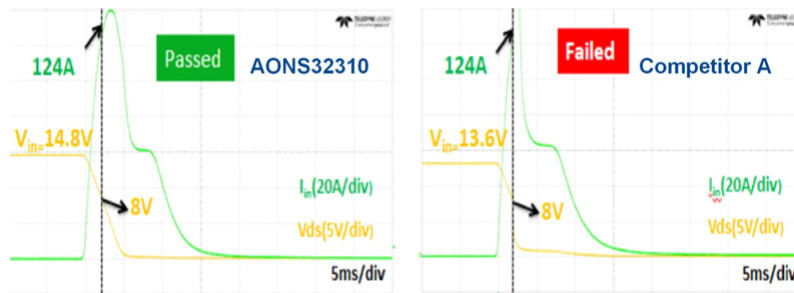

Click image to enlarge

Figure 4. Comparison of Start-up Waveform with No Load, same 70mF  $C_L$

Figure 5 replicates a worst-case condition where the MOSFETs are on and at the thermal equilibrium of 100°C. There is a reset where the hot-swap controller has to turn back on where the MOSFETs are under elevated temperature (100°C).

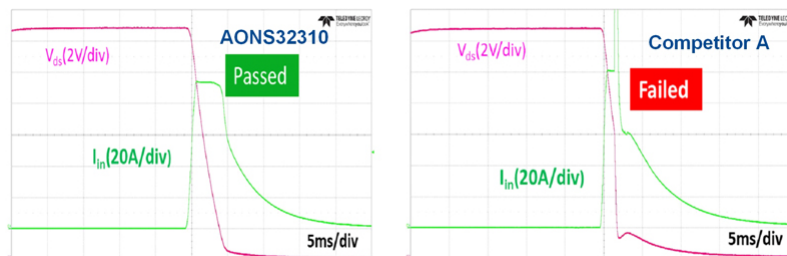

Click image to enlarge


Figure 5. Comparison of Start-up Waveform with No Load, same 50mF  $C_L$  Inside the 100°C Chamber Environment

These worst-case conditions demonstrate that AOS MOSFETs are robust for hot-swap applications compared to other competitors. Since the energy dissipated on the MOSFET is almost equal to the energy stored in the output  $C_L$ , AOS proposed to use the equation (3) to determine how robust in terms of SOA capability.

$$E_{dis} = \frac{1}{2} V_{in}^2 * C_L$$

On the other hand, if the same inrush current limit applies, the **AONS32100** will exhibit almost identical start-up waveforms as the competitor C but need to adjust the external  $C_{gate}$  and  $R_{gate}$ . In hot-swap applications, the  $C_{iss}$  will not affect the gate voltage during the linear mode. The MOSFET is already fully on and the minimum delay of gate voltage will not make a difference in the system's efficiency and performance.

Even the best-in-class MOSFET cannot withstand the fault condition, such as output short for seconds. Therefore, the hot-swap controller is required to shut down the MOSFET as soon as possible by sensing the current and voltage stress. The ADM1278 from Analog Devices is capable of both overcurrent and overpower protection. In an overpowering event, the controller will not turn off the MOSFET until the fault timer voltage hits the fault threshold 1V. The timer can be set according to the SOA of the MOSFET, which gives the designer the flexibility to choose the MOSFET that fits the system requirements and avoids the unnecessary shut down during the start-up and transient events. Figure 6 shows a series of OCP and OPP events based on the AOS evaluation board. It can be seen from the waveforms that the AONS32100 can withstand 42A/9V for more than 20ms in linear operation modes during short circuit fault in the worst-case scenario.

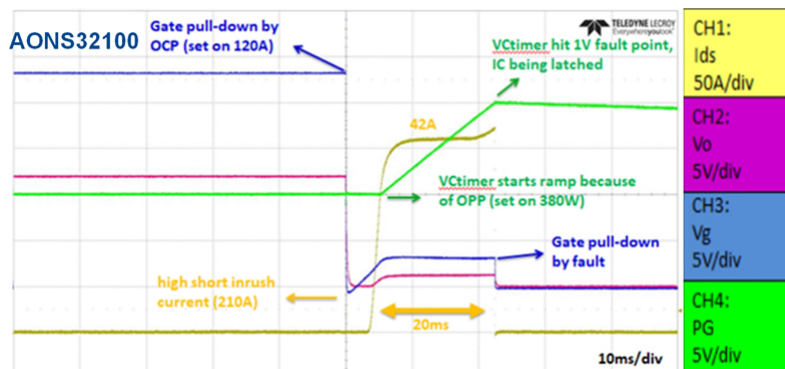

Click image to enlarge

Figure 6. Short-Circuit Conditions and Protections

Selecting a robust MOSFET is essential to hot-swap applications where failure even during worst-case conditions is essential for high availability. The high SOA and lower  $R_{dson}$  contribute to higher efficiency enabling the system to be more robust capability.

Alpha and Omega Semiconductor